

# Probability Hardware Project

## Random Number Generator

Name:Dikshant Khandelwal

Roll no:CS22BTECH11017

**Abstract—Here, we have made a Random Number Generator using shift registers.**

### COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K $\Omega$	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE I  
COMPONENTS USED

### PROCEDURE

- 1) We connect the 555 timer circuit to generate a Square Waveform Output according to figure 1

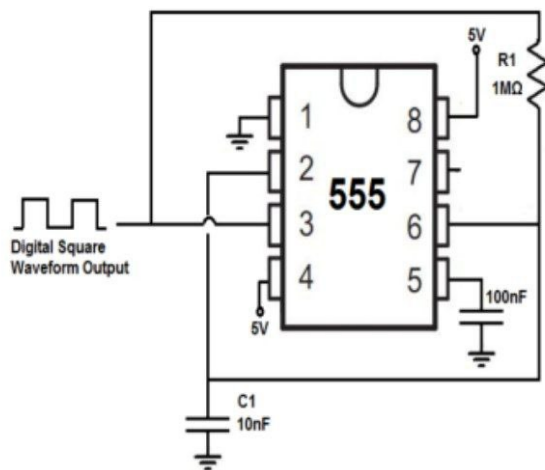


Fig. 1. 555 timer circuit

- 2) Then, the Square Waveform generated from 555 timer circuit is provided to D-Flip flops
- 3) Now, the circuit for shift registers is made using 4 D-Flip flops. So, we use two 7474 ICs.

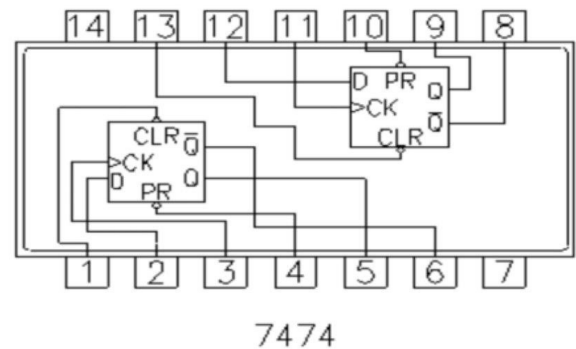


Fig. 2. Connection in 7474 IC

- 4) We then connect the XOR gate (7486 IC) to the system of D-Flip flops (shift register) according to the figure 3

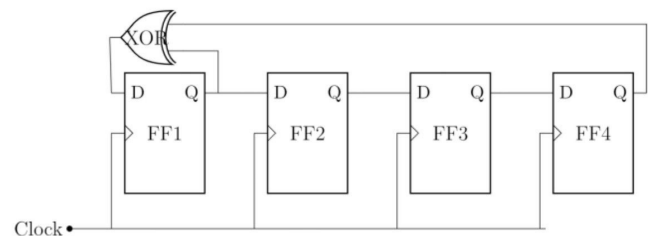


Fig. 3. Connection in XOR gate

- 5) Then, we connect the decoder (7447 IC) and connect its A,B,C,D with  $Q_0, Q_1, Q_2, Q_3$  (outputs of the D-Flip flops) respectively as per the figure 4
- 6) The seven segmented display is then connected with the decoder (7447 IC) according to the table 5 and the figure 6



Fig. 4. Connection in Decoder gate

7447	$\bar{a}$	$\bar{b}$	$\bar{c}$	$\bar{d}$	$\bar{e}$	$\bar{f}$	$\bar{g}$
Display	a	b	c	d	e	f	g

Fig. 5. Connection of seven segmented display with decoder

- 7) Finally, We connect all the independent parts with each other and then connect the circuit to the power source

#### OUTPUT

We get continuously changing digits on the seven segment display. The Output is shown in figures 7,8 and 9

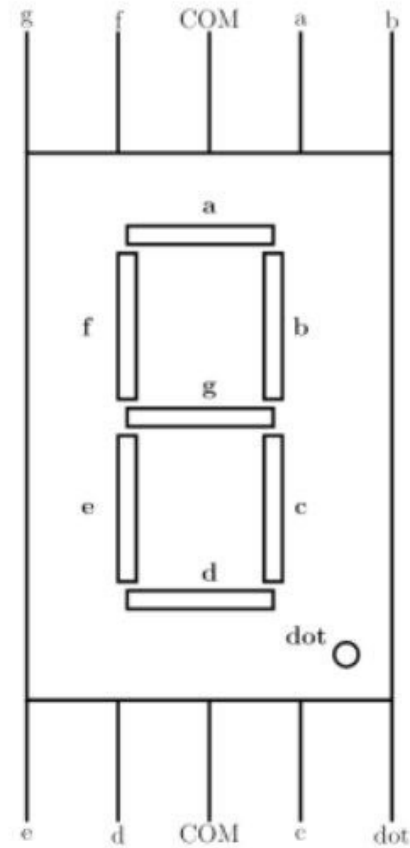


Fig. 6. Seven segmented display

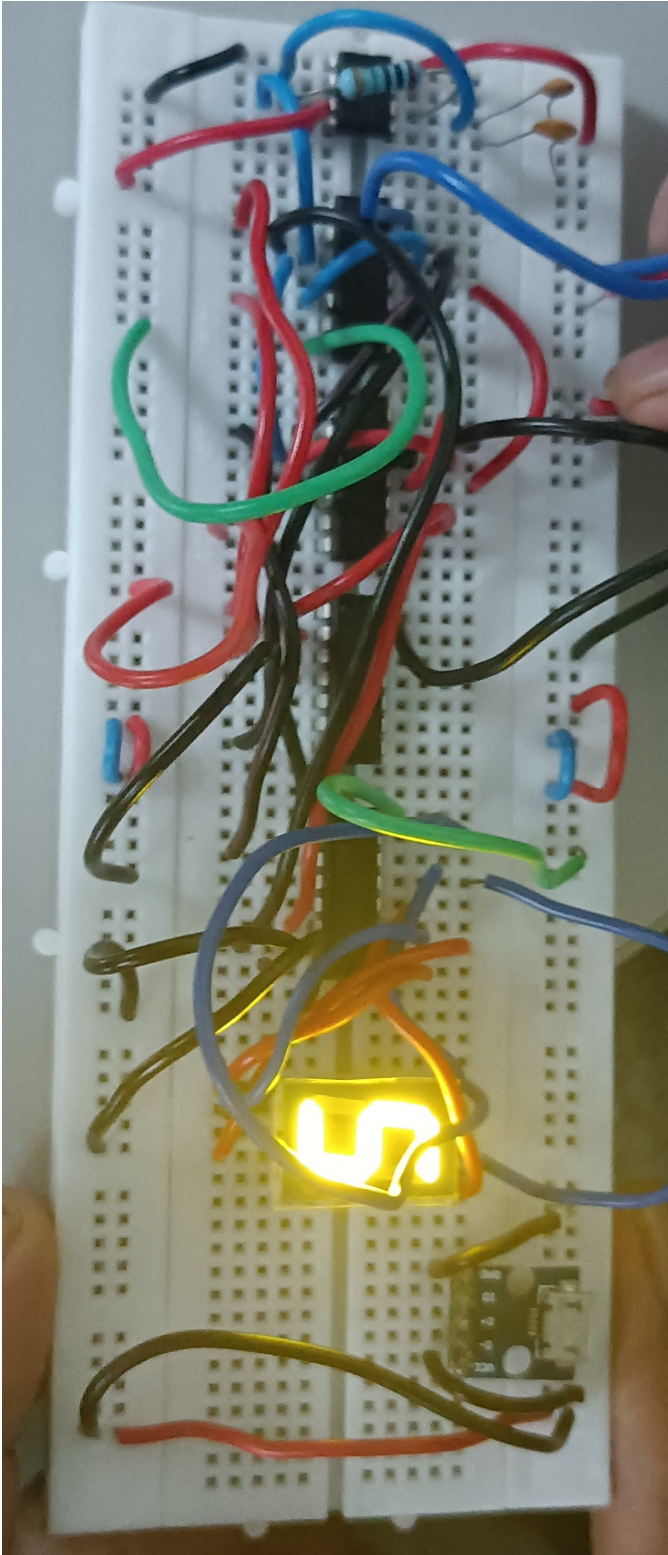


Fig. 7. Output1

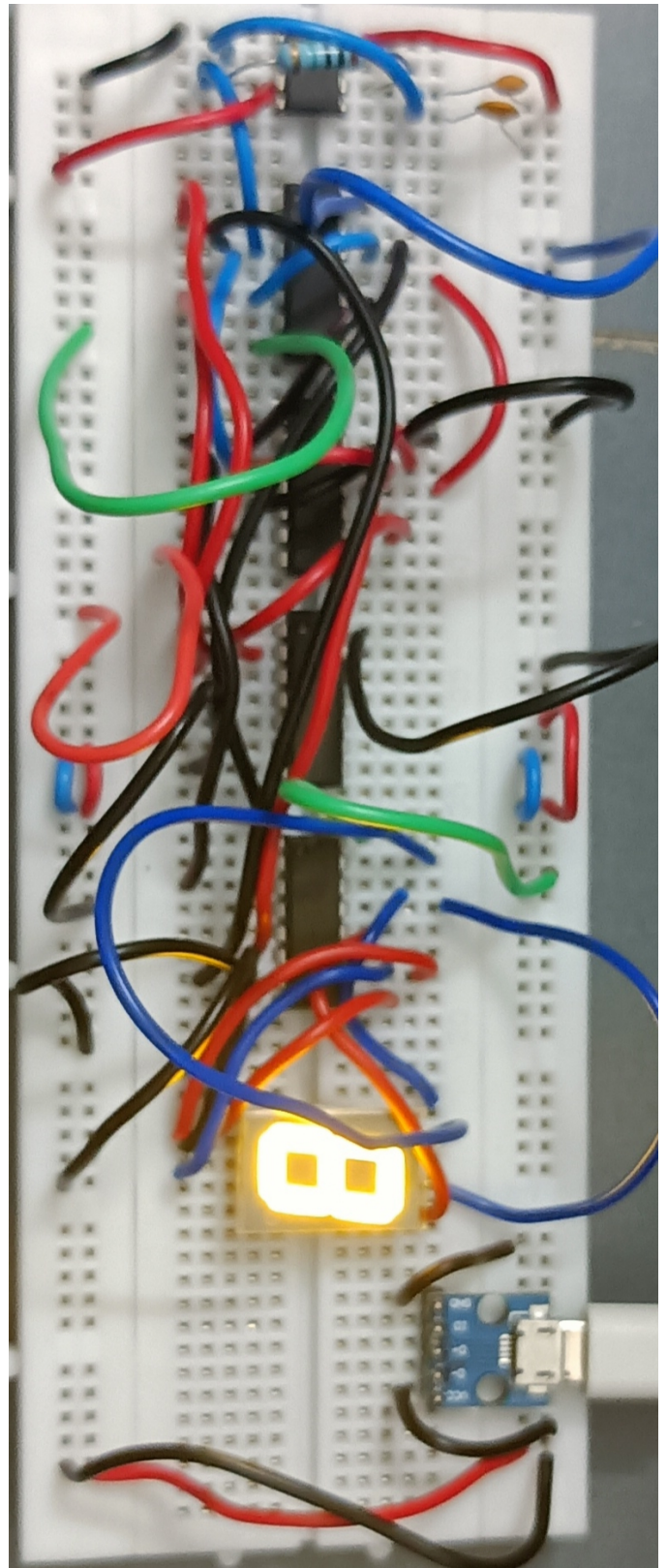


Fig. 8. Output2



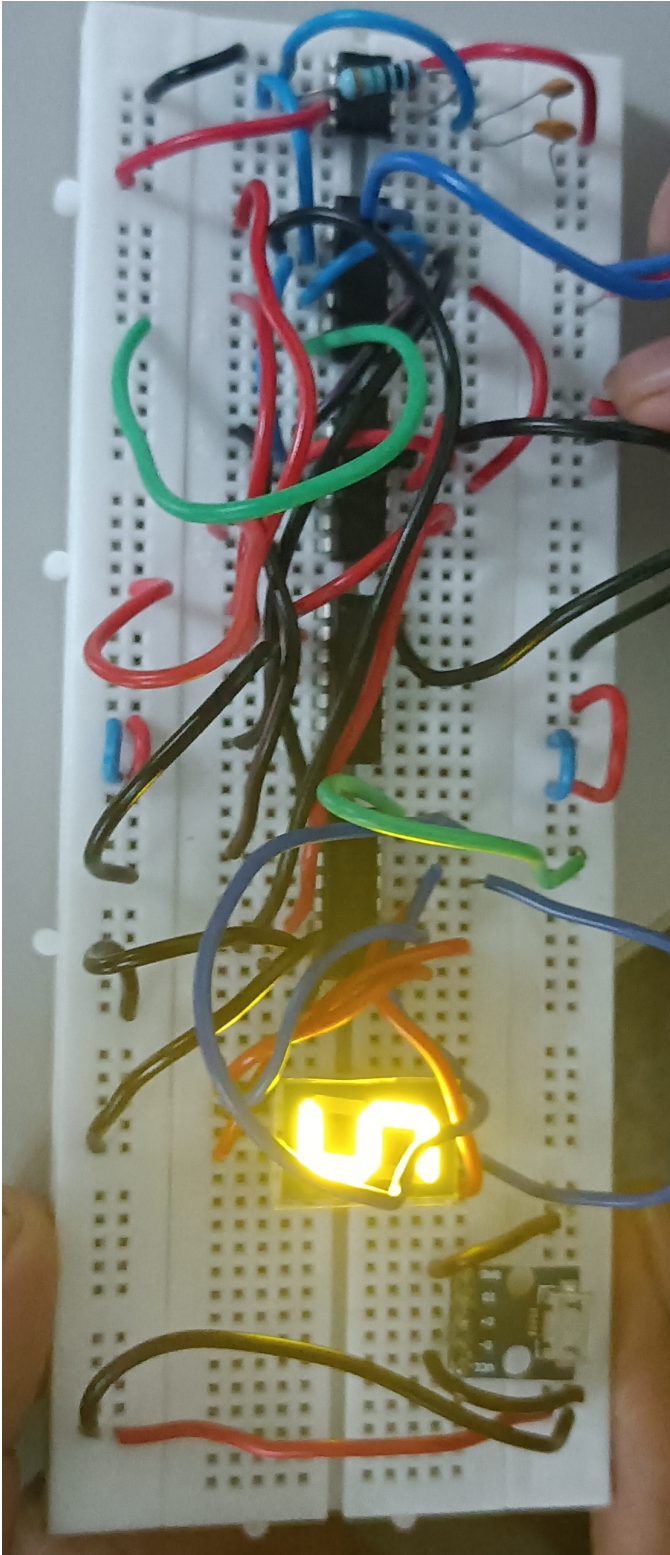


Fig. 9. Output3